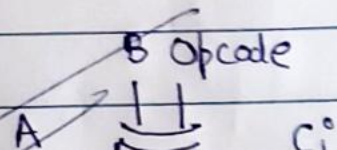


2. For the implementation of 8-bit adder/subtractor we have used 8-1 bit adder/subtractor for each bit of the no. We have used a input called as opcode which is 0 and 1 for addition and subtraction respectively.

Now it is not always true whether we can represent addition/subtraction of 2 numbers as a 8 bit number and this condition is called overflow in which our answer will come out to be incorrect.

We have given an output variable which is 1 when the input there is overflow condition and in most case it is 0.

~~1-bit adder/subtractor.~~



1 bit adder.

| a | b | Cin | sum | Count |
|---|---|-----|-----|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Sum:

| | AB | 00 | 01 | 11 | 10 |
|----------------|----|----|----|----|----|
| C _i | 0 | 0 | 1 | 0 | 1 |
| | 1 | 1 | 0 | 1 | 0 |

$$\rightarrow \text{Sum} = C_i \oplus A \oplus B$$

Count:

| | AB | 00 | 01 | 11 | 10 |
|----------------|----|----|----|----|----|
| C _i | 0 | 0 | 0 | 1 | 0 |
| | 1 | 0 | 1 | 1 | 1 |


$$\rightarrow C_o = C_i \cdot A + C_i \cdot B + A \cdot B$$

→ Description:

① We have designed first a normal 1 bit adder then, ~~A+B~~
 $A-B = A + (2's \text{ comp } B) = A + (\text{inversion of } B) + 1 = A + (\text{inversion of } B) + 1$

Now for the inversion we have used a XOR gate

⇒ whenever op code = 1 ⇒ invert else don't invert

| B | opcode | B _{final} | | B opcode |
|---|--------|--------------------|---|--|
| 0 | 0 | 0 | | 11 |
| 0 | 1 | 1 | ? |  |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | B _{final} |

② To add 1 to the whole answer we have given the Cin of first 1 bit adder as opcode so that whenever opcode = 1 we, to find 2's complement we can add 1 to inversion

$$C_{in,0} = \text{opcode}$$

③ whenever C_{in} for last bit is not equal to C_{out} for the last bit we get an overflow

| $C_{in,n}$ | $C_{out,n}$ | overflow |
|------------|-------------|----------|
| 0 | 0 | 0 |
| 1 | 1 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |

