 


Carry look ahead-Adder

Need For carry look ahead adders

- In case of a ripple carry adder, to carry out a sum of a particular bit we need C_{in} which is the carry from previous bit and similarly for the carry-in from previous bit we require its sum, which again require the sum of previous bit.
- So we can't find the sum of any 2 bit until we find the sum of all the previous bits and their carry. So there is a large time delay as all the bits sum is dependent on previous bit.
- The solution for this problem is:-
 - a) Either use a very fast gate to carry out the sum of two bit but again it will increase cost and also there is a limit to how much we can reduce time.
 - b) Or increase the complexity of the circuit to be able to independently find the sum of 2 bit by using some formulas.

Carry look Ahead adder



A	B	C_i	C_{i+1}	Type of carry
0	0	0	0	None
0	0	1	0	None
0	1	0	0	None
0	1	1	1	Propagate
1	0	0	0	None
1	0	1	1	Propagate
1	1	0	1	Generate
1	1	1	1	Generate / Propagate

We define 2 variable as carry generate G_i and carry propagate P_i then,

$$P_i = A_i \oplus B_i$$

$$G_i = A_i \cdot B_i$$

The sum and carry output can be expressed as

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i \cdot C_i$$

$G_i \rightarrow$ carry generate, which produce 1 if both A_i, B_i are 1 regardless of C_i

$P_i \rightarrow$ carry propagate, it is used to propagate carry from C_i to C_{i+1}


Now we can recursively fill the C_i from previous assignment of bits

C-in is carry input
assign

$$\begin{aligned}
 C_1 &= g_0 \vee (p_0 \& c_{in}) \\
 C_2 &= g_1 \vee (p_1 \& g_0) \vee (p_1 \& p_0 \& c_{in}) \\
 C_3 &= g_2 \vee (p_2 \& g_1) \vee (p_2 \& p_1 \& g_0) \vee (p_2 \& p_1 \& p_0 \& c_{in}) \\
 C_4 &= g_3 \vee (p_3 \& g_2) \vee (p_3 \& p_2 \& g_1) \vee (p_3 \& p_2 \& p_1 \& g_0) \vee \\
 &\quad (p_3 \& p_2 \& p_1 \& p_0 \& c_{in}) \\
 C_5 &= g_4 \vee (p_4 \& g_3) \vee (p_4 \& p_3 \& g_2) \vee (p_4 \& p_3 \& p_2 \& g_1) \vee \\
 &\quad (p_4 \& p_3 \& p_2 \& p_1 \& g_0) \vee \\
 &\quad (p_4 \& p_3 \& p_2 \& p_1 \& p_0 \& c_{in}) \\
 C_6 &= \dots \\
 C_7 &= \dots \\
 C_8 &= \dots
 \end{aligned}$$

now we can see the pattern, since the Boolean exp. for each carry output as the sum of product so this can be implemented with 1 level of AND gates followed by an OR gate.

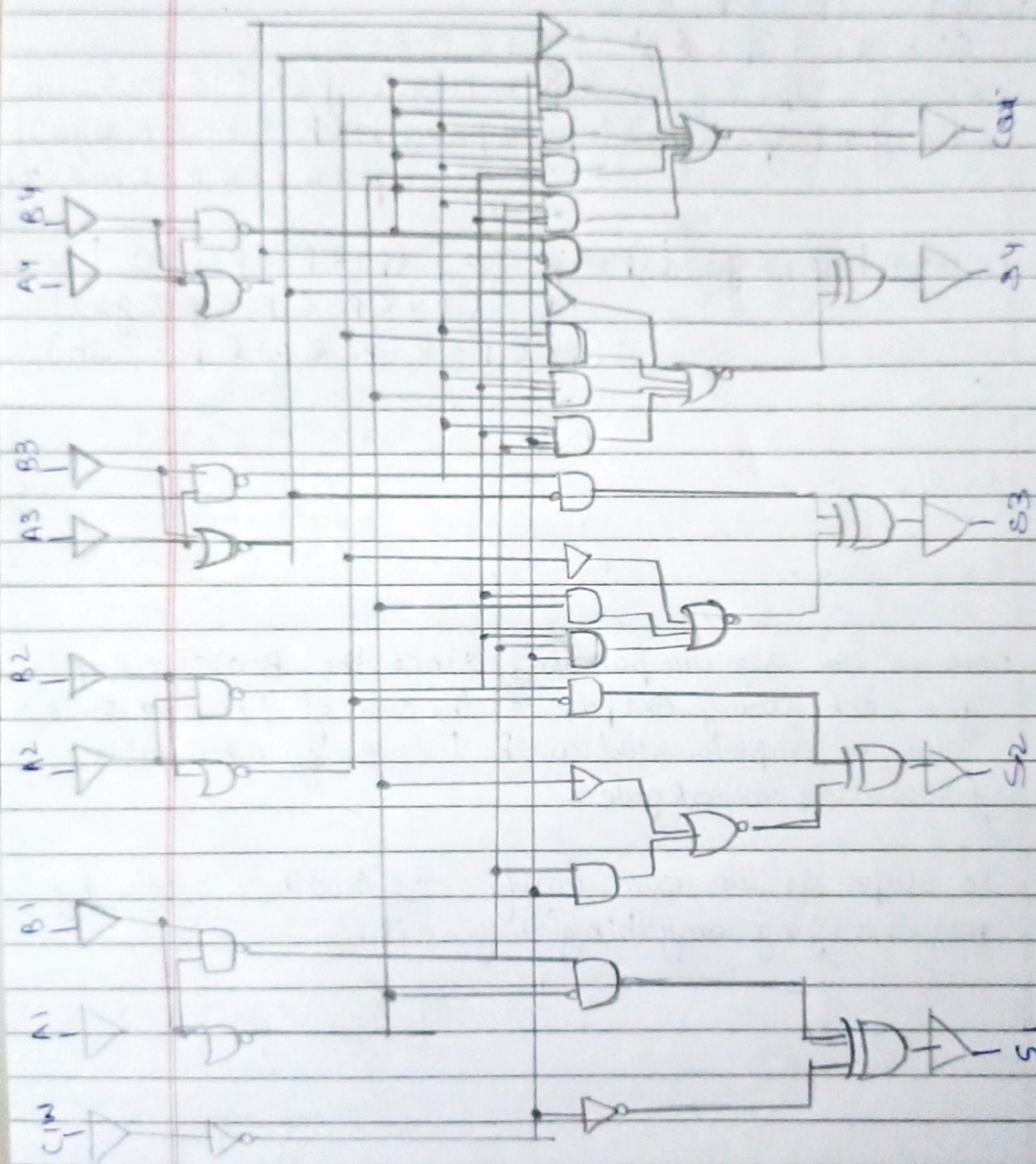→ To scale it we can easily add another adder by not changing anything before it.



Explanation

- ∴ The 4 bit parallel adder can be implemented with carry look ahead adder. to increase the speed of binary addition. For each sum-output 2 XOR gates are required one to generate P_i and ~~other~~ the AND gate gives G_i .
- ∴ Hence, in 2 gate level we can generate P_i and G_i .
- The carry look ahead generator allows the P and G signal to propagate after they settle into their steady state values and produces the output carries at a delay of 2 levels of gates.
- ∴ we get all the sum at same time and not one after another.